

Jonathan Sumner

Lab 4 – Transfer Function

EEET-332.01 – Signals, Systems, and
Transformers Lab

Due Date: 10/06/2024

Lab 4

Section 1 $H=V_{out}/V_{in}$

```
1  syms s R1 R2 C
2  Zc = 1/(s*C)
3  Zs = simplifyFraction(R2 + Zc)
4  H = simplifyFraction(Zs/(R1+Zs))
5  R1 = 4; R2 = 2; C = 3;
6  H = subs(H)
```

$Z_c =$

$$\frac{1}{Cs}$$

$Z_s =$

$$\frac{CR_2s + 1}{Cs}$$

$H =$

$$\frac{CR_2s + 1}{CR_1s + CR_2s + 1}$$

$H =$

$$\frac{6s + 1}{18s + 1}$$

Section 2 Impulse and Step

```
7 [sysNum, sysDen] = numden(H)
8 num = sym2poly(sysNum)
9 den = sym2poly(sysDen)
10
11 HTF = tf(num,den)
12
13 impulse(HTF)
14
15 roots(den)
16 pole(HTF)
17 pzmap(HTF)
18
```

sysNum = $6s + 1$

sysDen = $18s + 1$

num = 1×2
6 1

den = 1×2
18 1


HTF =

$$\frac{6s + 1}{18s + 1}$$

Continuous-time transfer function.

[Model Properties](#)


Impulse Response

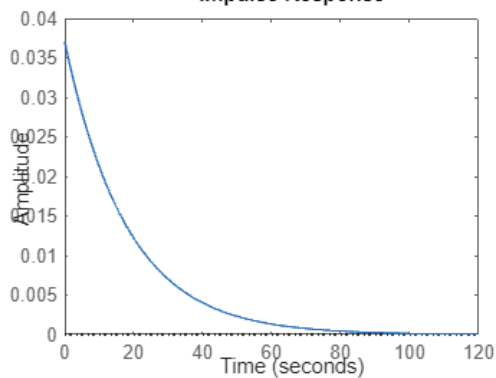


ans = -0.0556

ans = -0.0556

Pole-Zero Map

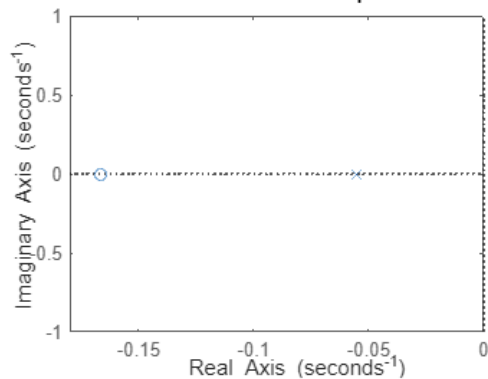

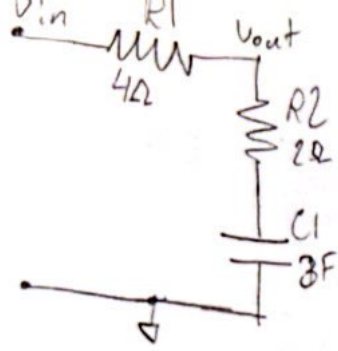

$$H = \frac{V_{out}}{V_{in}} = \frac{Z_{R2}}{Z_{R1} + Z_{R2} + Z_{C1}}$$

$$Z_{R1} = R1$$

$$Z_{R2} = R2$$

$$Z_{C1} = \frac{1}{sC1}$$

$$Z_s = Z_{R2} + Z_{C1} = \frac{C(R2)s + 1}{Cs}$$

$$H = \frac{Z_s}{Z_{R1} + Z_s} = \frac{C(R2)s + 1}{C(R1) + C(R2)s + 1} = \frac{3(2)s + 1}{3(4)s + 3(2)s + 1} = \frac{6s + 1}{12s + 6s + 1} = \boxed{\frac{6s + 1}{18s + 1}}$$

Signals Systems and Transforms
EEET-332
Lab 4

Report:



Create your own cover page.

Submit your cover page, the requested solutions and screenshots from sections 1 and 2, and this sign-off sheet.



Sign-offs

Name Jonathan Sumner



Section 3: Transfer function by hand and MATLAB

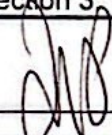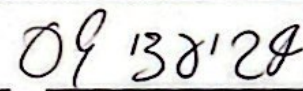	
Signature	Date

Section 4-1: Impulse, poles and pzmap

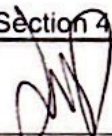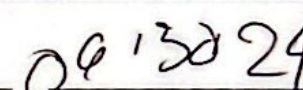	
Signature	Date

Section 4-2: Step Response (underdamped and critical/overdamped)

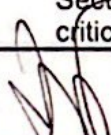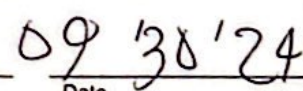	
Signature	Date